




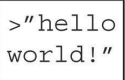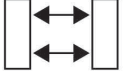
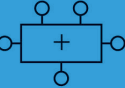
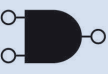
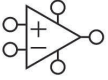

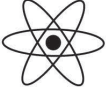
Chapter 2

Digital Design and Computer Architecture, 2nd Edition

David Money Harris and Sarah L. Harris

Chapter 2 :: Topics


- Introduction
- Boolean Equations
- Boolean Algebra
- From Logic to Gates
- Multilevel Combinational Logic
- X's and Z's, Oh My
- Karnaugh Maps
- Combinational Building Blocks
- Timing

Application Software	
Operating Systems	
Architecture	
Micro-architecture	
Logic	
Digital Circuits	
Analog Circuits	
Devices	
Physics	

Introduction

A logic circuit is composed of:

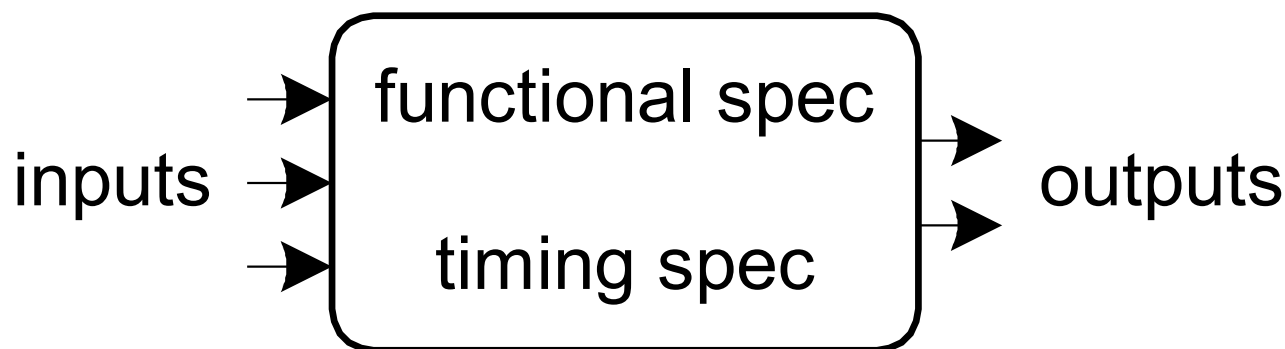- Inputs
- Outputs
- Functional specification
- Timing specification




Circuits

- **Nodes**

- Inputs: A, B, C
- Outputs: Y, Z
- Internal: $n1$


- **Circuit elements**

- $E1, E2, E3$
- Each a circuit

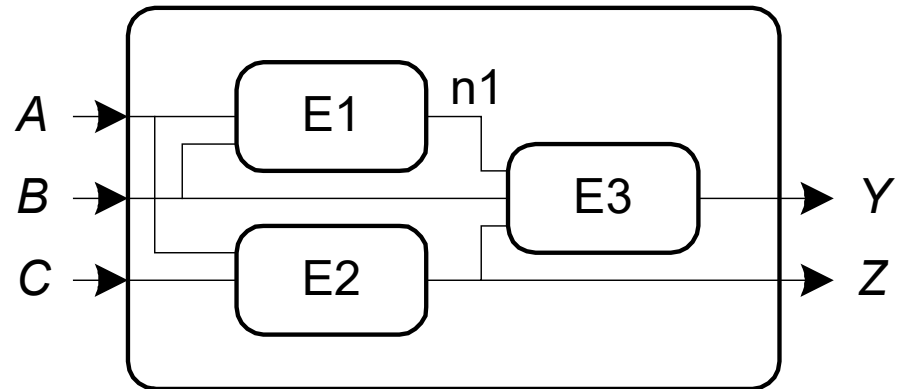


Types of Logic Circuits

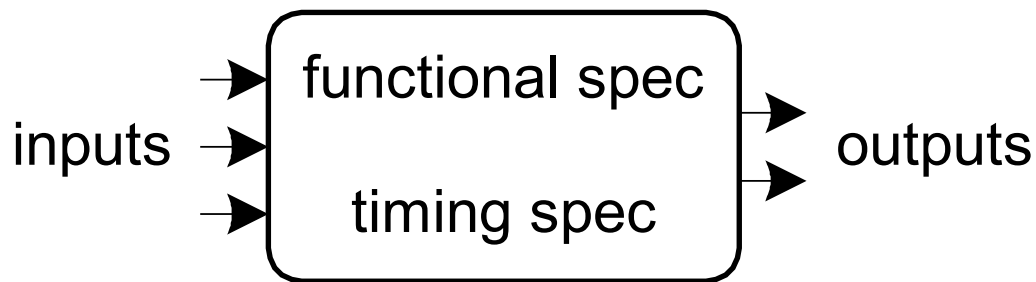- **Combinational Logic**
 - Memoryless
 - Outputs determined by current values of inputs
- **Sequential Logic**
 - Has memory
 - Outputs determined by previous and current values of inputs



Rules of Combinational Composition

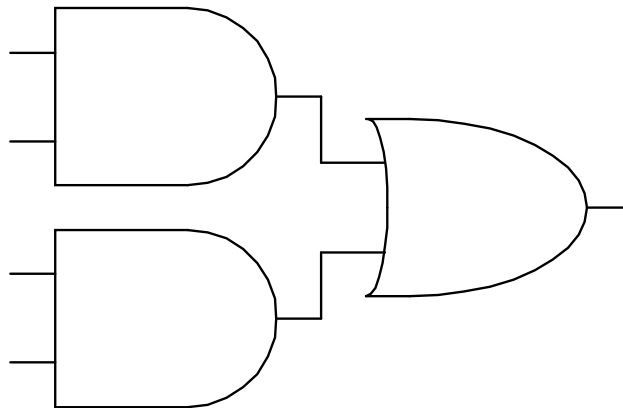
- Every element is combinational
- Every node is either an input or connects to *exactly one* output
- The circuit contains no cyclic paths
- **Example:**



Boolean Equations

- Functional specification of outputs in terms of inputs

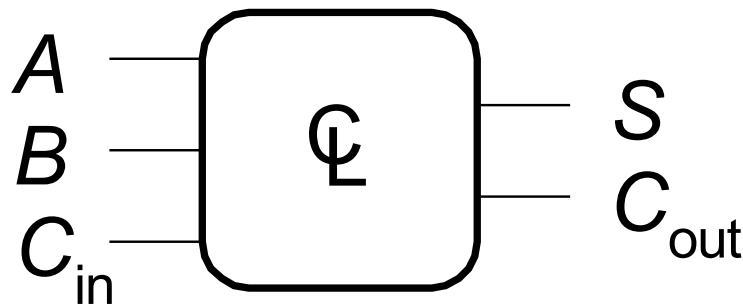- Example:** $S = F(A, B, C_{in})$
 $C_{out} = F(A, B, C_{in})$



$$S = A \oplus B \oplus C_{in}$$
$$C_{out} = AB + AC_{in} + BC_{in}$$

Some Definitions

- **Complement:** variable with a bar over it
 $\bar{A}, \bar{B}, \bar{C}$
- **Literal:** variable or its complement
 $A, \bar{A}, B, \bar{B}, C, \bar{C}$
- **Implicant:** product of literals
 $ABC, \bar{A}C, BC$
- **Minterm:** product that includes all input variables
 $ABC, \bar{A}\bar{B}\bar{C}, ABC$
- **Maxterm:** sum that includes all input variables
 $(A+B+C), (\bar{A}+B+\bar{C}), (\bar{A}+\bar{B}+C)$



Sum-of-Products (SOP) Form

- All Boolean equations can be written in SOP form
- Each row has a **minterm**

<i>A</i>	<i>B</i>	<i>Y</i>	minterm	minterm name
0	0		$\overline{A} \overline{B}$	m_0
0	1		$\overline{A} B$	m_1
1	0		$A \overline{B}$	m_2
1	1		$A B$	m_3

Sum-of-Products (SOP) Form

- All Boolean equations can be written in SOP form
- Each row has a **minterm**
- A minterm is a **product** (AND) of literals
- Each minterm is **TRUE** for that row (and only that row)

<i>A</i>	<i>B</i>	<i>Y</i>	minterm	minterm name
0	0		$\overline{A} \overline{B}$	m_0
0	1		$\overline{A} B$	m_1
1	0		$A \overline{B}$	m_2
1	1		$A B$	m_3

Sum-of-Products (SOP) Form

- All Boolean equations can be written in SOP form
- Each row has a **minterm**
- A minterm is a **product** (AND) of literals
- Each minterm is **TRUE** for that row (and only that row)
- Form function by **ORing minterms** where **output is 1**
- Thus, a **sum** (OR) of **products** (AND terms)

<i>A</i>	<i>B</i>	<i>Y</i>	minterm	minterm name
0	0	0	$\overline{A} \overline{B}$	m_0
0	1	1	$\overline{A} B$	m_1
1	0	0	$A \overline{B}$	m_2
1	1	1	$A B$	m_3

$$Y = F(A, B) = \overline{A}B + AB$$

Sum-of-Products (SOP) Form

- All equations can be written in SOP form
- Each row has a **minterm**
- A minterm is a **product** (AND) of literals
- Each minterm is **TRUE** for that row (and only that row)
- Form function by **ORing minterms** where **output is 1**
- Thus, a **sum** (OR) of **products** (AND terms)

<i>A</i>	<i>B</i>	<i>Y</i>	minterm	minterm name
0	0	0	$\overline{A} \overline{B}$	m_0
0	1	1	$\overline{A} B$	m_1
1	0	0	$A \overline{B}$	m_2
1	1	1	$A B$	m_3

$$Y = F(A, B) = \overline{A}B + AB = \Sigma(1, 3)$$

Product-of-Sums (POS) Form

- All Boolean equations can be written in POS form
- Each row has a **maxterm**

<i>A</i>	<i>B</i>	<i>Y</i>	maxterm	maxterm name
0	0		$A + B$	M_0
0	1		$A + \overline{B}$	M_1
1	0		$\overline{A} + B$	M_2
1	1		$\overline{A} + \overline{B}$	M_3

Product-of-Sums (POS) Form

- All Boolean equations can be written in POS form
- Each row has a **maxterm**
- A maxterm is a **sum** (OR) of literals
- Each maxterm is **FALSE** for that row (and only that row)

<i>A</i>	<i>B</i>	<i>Y</i>	maxterm	maxterm name
0	0		$A + B$	M_0
0	1		$A + \overline{B}$	M_1
1	0		$\overline{A} + B$	M_2
1	1		$\overline{A} + \overline{B}$	M_3

Product-of-Sums (POS) Form

- All Boolean equations can be written in POS form
- Each row has a **maxterm**
- A maxterm is a **sum** (OR) of literals
- Each maxterm is **FALSE** for that row (and only that row)
- Form function by **ANDing maxterms** where **output is 0**
- Thus, a **product** (AND) of **sums** (OR terms)

A	B	Y	maxterm	maxterm name
0	0	0	$A + B$	M_0
0	1	1	$A + \overline{B}$	M_1
1	0	0	$\overline{A} + B$	M_2
1	1	1	$\overline{A} + \overline{B}$	M_3

$$Y = F(A, B) = (A + B) \bullet (A + \overline{B})$$

Product-of-Sums (POS) Form

- All Boolean equations can be written in POS form
- Each row has a **maxterm**
- A maxterm is a **sum** (OR) of literals
- Each maxterm is **FALSE** for that row (and only that row)
- Form function by **ANDing maxterms** where **output is 0**
- Thus, a **product** (AND) of **sums** (OR terms)

A	B	Y	maxterm	maxterm name
0	0	0	$A + B$	M_0
0	1	1	$A + \overline{B}$	M_1
1	0	0	$\overline{A} + B$	M_2
1	1	1	$\overline{A} + \overline{B}$	M_3

$$Y = F(A, B) = (A + B)(A + \overline{B}) = \Pi(0, 2)$$

Boolean Equations Example

- You are going to the cafeteria for lunch
 - You won't eat lunch ($E = 0$)
 - If it's not open ($O = 0$) or
 - If they only serve corndogs ($C = 1$)
- Write a truth table for determining if you will eat lunch (E).

O	C	E
0	0	
0	1	
1	0	
1	1	

Boolean Equations Example

- You are going to the cafeteria for lunch
 - You won't eat lunch ($E = 0$)
 - If it's not open ($O = 0$) or
 - If they only serve corndogs ($C = 1$)
- Write a truth table for determining if you will eat lunch (E).

O	C	E
0	0	0
0	1	0
1	0	1
1	1	0

SOP & POS Form

- SOP** – sum-of-products

O	C	E	minterm
0	0		$\overline{O} \overline{C}$
0	1		$\overline{O} C$
1	0		$O \overline{C}$
1	1		$O C$

- POS** – product-of-sums

O	C	E	maxterm
0	0		$O + C$
0	1		$O + \overline{C}$
1	0		$\overline{O} + C$
1	1		$\overline{O} + \overline{C}$

SOP & POS Form

- SOP** – sum-of-products

O	C	E	minterm
0	0	0	$\overline{O} \overline{C}$
0	1	0	$\overline{O} C$
1	0	1	$O \overline{C}$
1	1	0	$O C$

$$E = O\overline{C}$$

$$= \Sigma(2)$$

- POS** – product-of-sums

O	C	E	maxterm
0	0	0	$O + C$
0	1	0	$O + \overline{C}$
1	0	1	$\overline{O} + C$
1	1	0	$\overline{O} + \overline{C}$

$$E = (O + C)(O + \overline{C})(\overline{O} + \overline{C})$$

$$= \Pi(0, 1, 3)$$

Boolean Algebra

- Axioms and theorems to **simplify** Boolean equations
- Like regular algebra, but simpler: variables have only two values (1 or 0)
- **Duality** in axioms and theorems:
 - ANDs and ORs, 0's and 1's interchanged

Boolean Axioms

Number	Axiom	Name
A1	$B = 0 \text{ if } B \neq 1$	Binary Field
A2	$0 = \overline{1}$	NOT
A3	$0 \bullet 0 = 0$	AND/OR
A4	$1 \bullet 1 = 1$	AND/OR
A5	$0 \bullet 1 = 1 \bullet 0 = 0$	AND/OR

Boolean Axioms

Number	Axiom	Name
A1	$B = 0 \text{ if } B \neq 1$	Binary Field
A2	$0 = \bar{1}$	NOT
A3	$0 \bullet 0 = 0$	AND/OR
A4	$1 \bullet 1 = 1$	AND/OR
A5	$0 \bullet 1 = 1 \bullet 0 = 0$	AND/OR

Dual: Replace: \bullet with $+$
 0 with 1

Boolean Axioms

Number	Axiom	Dual	Name
A1	$B = 0 \text{ if } B \neq 1$	$B = 1 \text{ if } B \neq 0$	Binary Field
A2	$0 = \bar{1}$	$1 = \bar{0}$	NOT
A3	$0 \bullet 0 = 0$	$1 + 1 = 1$	AND/OR
A4	$1 \bullet 1 = 1$	$0 + 0 = 0$	AND/OR
A5	$0 \bullet 1 = 1 \bullet 0 = 0$	$1 + 0 = 0 + 1 = 1$	AND/OR

Dual: Replace: \bullet with $+$
 0 with 1



Boolean Theorems of One Variable

Number	Theorem	Name
T1	$B \bullet 1 = B$	Identity
T2	$B \bullet 0 = 0$	Null Element
T3	$B \bullet B = B$	Idempotency
T4	$\overline{\overline{B}} = B$	Involution
T5	$B \bullet \overline{B} = 0$	Complements

Boolean Theorems of One Variable

Number	Theorem	Name
T1	$B \bullet 1 = B$	Identity
T2	$B \bullet 0 = 0$	Null Element
T3	$B \bullet B = B$	Idempotency
T4	$\overline{\overline{B}} = B$	Involution
T5	$B \bullet \overline{B} = 0$	Complements

Dual: Replace: \bullet with $+$
 0 with 1

Boolean Theorems of One Variable

Number	Theorem	Dual	Name
T1	$B \bullet 1 = B$	$B + 0 = B$	Identity
T2	$B \bullet 0 = 0$	$B + 1 = 1$	Null Element
T3	$B \bullet B = B$	$B + B = B$	Idempotency
T4	$\overline{\overline{B}} = B$		Involution
T5	$B \bullet \overline{B} = 0$	$B + \overline{B} = 1$	Complements



Dual: Replace: \bullet with $+$
 0 with 1

T1: Identity Theorem

- $B \cdot 1 = B$
- $B + 0 = B$

T1: Identity Theorem

- $B \cdot 1 = B$
- $B + 0 = B$

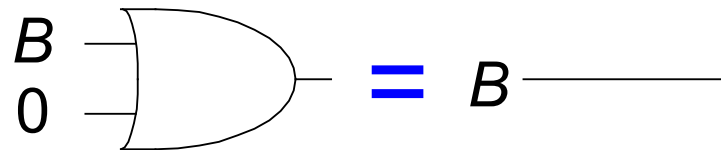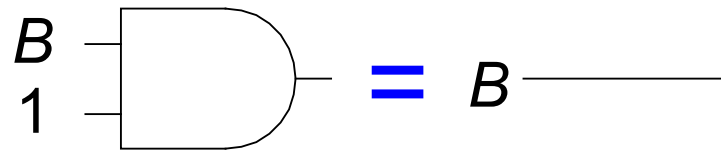



T2: Null Element Theorem

- $B \cdot 0 = 0$
- $B + 1 = 1$



T2: Null Element Theorem

- $B \cdot 0 = 0$
- $B + 1 = 1$

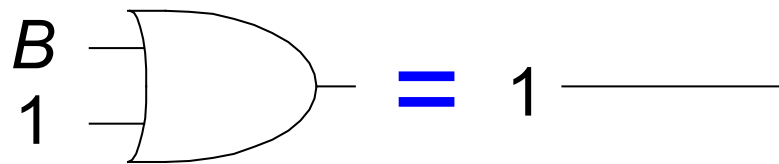
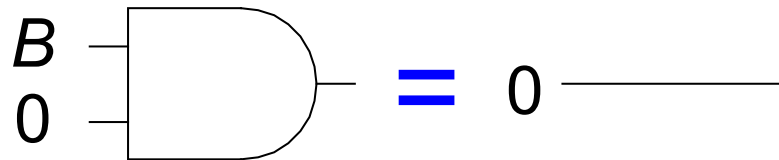


T3: Idempotency Theorem

- $B \cdot B = B$
- $B + B = B$

T3: Idempotency Theorem

- $B \cdot B = B$
- $B + B = B$

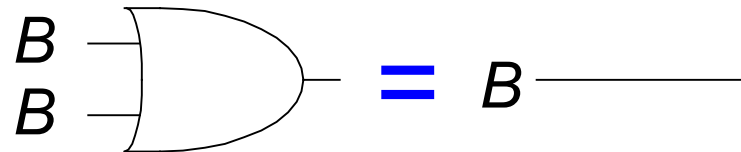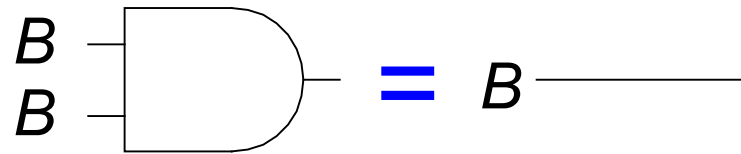


T4: Identity Theorem

- $\overline{\overline{B}} = B$

T4: Identity Theorem

- $\overline{\overline{B}} = B$


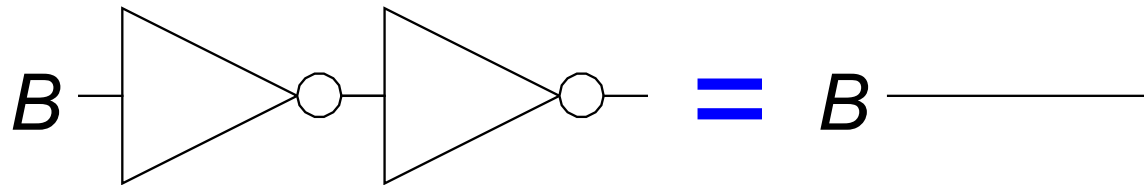


T5: Complement Theorem

- $B \cdot \overline{B} = 0$
- $B + \overline{B} = 1$

T5: Complement Theorem

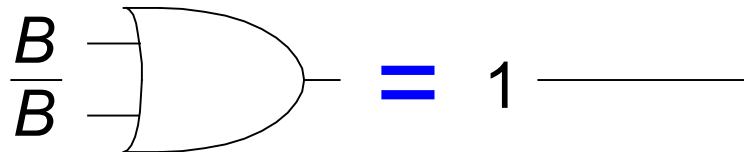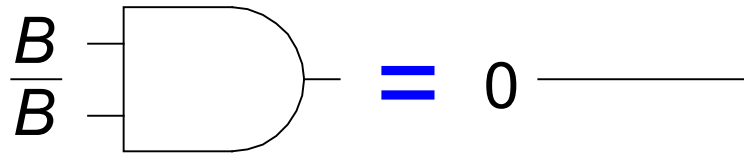- $B \cdot \overline{B} = 0$
- $B + \overline{B} = 1$



Recap: Basic Boolean Theorems

Number	Theorem	Dual	Name
T1	$B \bullet 1 = B$	$B + 0 = B$	Identity
T2	$B \bullet 0 = 0$	$B + 1 = 1$	Null Element
T3	$B \bullet B = B$	$B + B = B$	Idempotency
T4	$\overline{\overline{B}} = B$		Involution
T5	$B \bullet \overline{B} = 0$	$B + \overline{B} = 1$	Complements

Dual: Replace: \bullet with $+$
 0 with 1

Boolean Theorems of Several Vars

Number	Theorem	Name
T6	$B \bullet C = C \bullet B$	Commutativity
T7	$(B \bullet C) \bullet D = B \bullet (C \bullet D)$	Associativity
T8	$B \bullet (C + D) = (B \bullet C) + (B \bullet D)$	Distributivity
T9	$B \bullet (B + C) = B$	Covering
T10	$(B \bullet C) + (B \bullet \bar{C}) = B$	Combining
T11	$(B \bullet C) + (\bar{B} \bullet D) + (C \bullet D) = (B \bullet C) + (\bar{B} \bullet D)$	Consensus

Boolean Theorems of Several Vars

#	Theorem	Dual	Name
T6	$B \bullet C = C \bullet B$	$B + C = C + B$	Commutativity
T7	$(B \bullet C) \bullet D = B \bullet (C \bullet D)$	$(B + C) + D = B + (C + D)$	Associativity
T8	$B \bullet (C + D) = (B \bullet C) + (B \bullet D)$	$B + (C \bullet D) = (B + C) (B + D)$	Distributivity
T9	$B \bullet (B + C) = B$	$B + (B \bullet C) = B$	Covering
T10	$(B \bullet C) + (B \bullet \bar{C}) = B$	$(B + C) \bullet (B + \bar{C}) = B$	Combining
T11	$(B \bullet C) + (\bar{B} \bullet D) + (C \bullet D) = (B \bullet C) + (\bar{B} \bullet D)$	$(B + C) \bullet (\bar{B} + D) \bullet (C + D) = (B + C) \bullet (\bar{B} + D)$	Consensus

Dual: Replace: \bullet with $+$
 0 with 1

Boolean Theorems of Several Vars

#	Theorem	Dual	Name
T6	$B \bullet C = C \bullet B$	$B + C = C + B$	Commutativity
T7	$(B \bullet C) \bullet D = B \bullet (C \bullet D)$	$(B + C) + D = B + (C + D)$	Associativity
T8	$B \bullet (C + D) = (B \bullet C) + (B \bullet D)$	$B + (C \bullet D) = (B + C) (B + D)$	Distributivity
T9	$B \bullet (B + C) = B$	$B + (B \bullet C) = B$	Covering
T10	$(B \bullet C) + (B \bullet \bar{C}) = B$	$(B + C) \bullet (B + \bar{C}) = B$	Combining
T11	$(B \bullet C) + (\bar{B} \bullet D) + (C \bullet D) = (B \bullet C) + (\bar{B} \bullet D)$	$(B + C) \bullet (\bar{B} + D) \bullet (C + D) = (B + C) \bullet (\bar{B} + D)$	Consensus

Warning: T8' differs from traditional algebra:
OR (+) distributes over AND (\bullet)

Boolean Theorems of Several Vars

#	Theorem	Dual	Name
T6	$B \bullet C = C \bullet B$	$B + C = C + B$	Commutativity
T7	$(B \bullet C) \bullet D = B \bullet (C \bullet D)$	$(B + C) + D = B + (C + D)$	Associativity
T8	$B \bullet (C + D) = (B \bullet C) + (B \bullet D)$	$B + (C \bullet D) = (B + C) (B + D)$	Distributivity
T9	$B \bullet (B + C) = B$	$B + (B \bullet C) = B$	Covering
T10	$(B \bullet C) + (B \bullet \bar{C}) = B$	$(B + C) \bullet (B + \bar{C}) = B$	Combining
T11	$(B \bullet C) + (\bar{B} \bullet D) + (C \bullet D) = (B \bullet C) + (\bar{B} \bullet D)$	$(B + C) \bullet (\bar{B} + D) \bullet (C + D) = (B + C) \bullet (\bar{B} + D)$	Consensus

How do we prove these are true?

How to Prove

- **Method 1:** Perfect induction
- **Method 2:** Use other theorems and axioms to simplify the equation
 - Make one side of the equation look like the other

Proof by Perfect Induction

- Also called: **proof by exhaustion**
- Check every possible input value
- If the two expressions produce the same value for every possible input combination, the expressions are equal

Example: Proof by Perfect Induction

Number	Theorem	Name
T6	$B \bullet C = C \bullet B$	Commutativity

<i>B</i>	<i>C</i>	<i>BC</i>	<i>CB</i>
0	0		
0	1		
1	0		
1	1		

Example: Proof by Perfect Induction

Number	Theorem	Name
T6	$B \bullet C = C \bullet B$	Commutativity

<i>B</i>	<i>C</i>	<i>BC</i>	<i>CB</i>
0	0	0	0
0	1	0	0
1	0	0	0
1	1	1	1

Boolean Theorems of Several Vars

#	Theorem	Dual	Name
T6	$B \bullet C = C \bullet B$	$B + C = C + B$	Commutativity
T7	$(B \bullet C) \bullet D = B \bullet (C \bullet D)$	$(B + C) + D = B + (C + D)$	Associativity
T8	$B \bullet (C + D) = (B \bullet C) + (B \bullet D)$	$B + (C \bullet D) = (B + C) (B + D)$	Distributivity
T9	$B \bullet (B + C) = B$	$B + (B \bullet C) = B$	Covering
T10	$(B \bullet C) + (B \bullet \bar{C}) = B$	$(B + C) \bullet (B + \bar{C}) = B$	Combining
T11	$(B \bullet C) + (\bar{B} \bullet D) + (C \bullet D) = (B \bullet C) + (\bar{B} \bullet D)$	$(B + C) \bullet (\bar{B} + D) \bullet (C + D) = (B + C) \bullet (\bar{B} + D)$	Consensus

How do we prove these are true?

T7: Associativity

Number	Theorem	Name
T7	$(B \bullet C) \bullet D = B \bullet (C \bullet D)$	Associativity

T8: Distributivity

Number	Theorem	Name
T8	$B \bullet (C + D) = (B \bullet C) + (B \bullet D)$	Distributivity

T9: Covering

Number	Theorem	Name
T9	$B \bullet (B+C) = B$	Covering

T9: Covering

Number	Theorem	Name
T9	$B \bullet (B+C) = B$	Covering

Prove true by:

- **Method 1:** Perfect induction
- **Method 2:** Using other theorems and axioms

T9: Covering

Number	Theorem	Name
T9	$B \bullet (B+C) = B$	Covering

Method 1: Perfect Induction

B	C	$(B+C)$	$B(B+C)$
0	0		
0	1		
1	0		
1	1		

T9: Covering

Number	Theorem	Name
T9	$B \bullet (B+C) = B$	Covering

Method 1: Perfect Induction

B	C	$(B+C)$	$B(B+C)$
0	0	0	0
0	1	1	0
1	0	1	1
1	1	1	1

T9: Covering

Number	Theorem	Name
T9	$B \bullet (B+C) = B$	Covering

Method 1: Perfect Induction

B	C	$(B+C)$	$B(B+C)$
0	0	0	0
0	1	1	0
1	0	1	1
1	1	1	1

T9: Covering

Number	Theorem	Name
T9	$B \bullet (B+C) = B$	Covering

Method 2: Prove true using other axioms and theorems.

T9: Covering

Number	Theorem	Name
T9	$B \bullet (B+C) = B$	Covering

Method 2: Prove true using other axioms and theorems.

$$\begin{aligned} B \bullet (B+C) &= B \bullet B + B \bullet C \\ &= \mathbf{B} + B \bullet C \\ &= B \bullet (1 + C) \\ &= B \bullet (\mathbf{1}) \\ &= B \end{aligned}$$

T8: Distributivity
T3: Idempotency
T8: Distributivity
T2: Null element
T1: Identity

T10: Combining

Number	Theorem	Name
T10	$(B \bullet C) + (B \bullet C) = B$	Combining

Prove true using other axioms and theorems:

T10: Combining

Number	Theorem	Name
T10	$(B \bullet C) + (B \bullet \overline{C}) = B$	Combining

Prove true using other axioms and theorems:

$$\begin{aligned} B \bullet C + B \bullet \overline{C} &= B \bullet (C + \overline{C}) && \text{T8: Distributivity} \\ &= B \bullet (1) && \text{T5': Complements} \\ &= B && \text{T1: Identity} \end{aligned}$$

T11: Consensus

Number	Theorem	Name
T11	$(B \bullet C) + (\bar{B} \bullet D) + (C \bullet D) = (B \bullet C) + (\bar{B} \bullet D)$	Consensus

Prove true using (1) perfect induction or (2) other axioms and theorems.

Boolean Theorems of Several Vars

#	Theorem	Dual	Name
T6	$B \bullet C = C \bullet B$	$B + C = C + B$	Commutativity
T7	$(B \bullet C) \bullet D = B \bullet (C \bullet D)$	$(B + C) + D = B + (C + D)$	Associativity
T8	$B \bullet (C + D) = (B \bullet C) + (B \bullet D)$	$B + (C \bullet D) = (B + C) (B + D)$	Distributivity
T9	$B \bullet (B + C) = B$	$B + (B \bullet C) = B$	Covering
T10	$(B \bullet C) + (B \bullet \bar{C}) = B$	$(B + C) \bullet (B + \bar{C}) = B$	Combining
T11	$(B \bullet C) + (\bar{B} \bullet D) + (C \bullet D) = (B \bullet C) + (\bar{B} \bullet D)$	$(B + C) \bullet (\bar{B} + D) \bullet (C + D) = (B + C) \bullet (\bar{B} + D)$	Consensus

Axioms and theorems are useful for *simplifying* equations.



Simplifying an Equation

Reducing an equation to the **fewest number of implicants**, where each implicant has the **fewest literals**

Simplifying an Equation

Reducing an equation to the **fewest number of implicants**, where each implicant has the **fewest literals**

Recall:

- **Implicant:** product of literals

$$\overline{A}BC, \overline{A}\overline{C}, BC$$

- **Literal:** variable or its complement

$$\overline{A}, A, \overline{B}, B, \overline{C}, C$$



Simplifying an Equation

Reducing an equation to the **fewest number of implicants**, where each implicant has the **fewest literals**

Recall:

- **Implicant:** product of literals

$\bar{A}BC, \bar{A}\bar{C}, BC$

- **Literal:** variable or its complement

$\bar{A}, A, \bar{B}, B, \bar{C}, C$

*Simplifying the equation is also called **minimizing** the equation*

Simplification methods

- **Distributivity (T8, T8')**
 $B(C+D) = BC + BD$
 $B + CD = (B + C)(B + D)$
- **Covering (T9')**
 $A + AP = A$
- **Combining (T10)**
 $\overline{P}A + PA = P$

Simplification methods

- **Distributivity (T8, T8')**
 $B(C+D) = BC + BD$
 $B + CD = (B+C)(B+D)$
- **Covering (T9')**
 $A + AP = A$
- **Combining (T10)**
 $\overline{PA} + PA = P$
- **Expansion**
 $P = \overline{PA} + PA$
 $A = A + AP$
- **Duplication**
 $A = A + A$



Simplification methods

- **Distributivity (T8, T8')**

$$B(C+D) = BC + BD$$

$$B + CD = (B + C)(B + D)$$
- **Covering (T9')**

$$A + AP = A$$
- **Combining (T10)**

$$P\bar{A} + PA = P$$
- **Expansion**

$$P = P\bar{A} + PA$$

$$A = A + AP$$
- **Duplication**

$$A = A + A$$
- **“Simplification” theorem**

$$P\bar{A} + A = P + A$$

$$PA + \bar{A} = P + \bar{A}$$

Proving the “Simplification” Theorem

“Simplification” theorem

$$PA + \bar{A} = P + \bar{A}$$

Method 1: $PA + \bar{A} = PA + (\bar{A} + \bar{A}P)$
 $= PA + P\bar{A} + \bar{A}$
 $= P(A + \bar{A}) + \bar{A}$
 $= P(1) + \bar{A}$
 $= P + \bar{A}$

T9' Covering

T6 Commutativity

T8 Distributivity

T5' Complements

T1 Identity

Proving the “Simplification” Theorem

“Simplification” theorem

$$PA + \bar{A} = P + \bar{A}$$

Method 2: $PA + \bar{A} = (\bar{A} + A)(\bar{A} + P)$
 $= 1(\bar{A} + P)$
 $= \bar{A} + P$

T8' Distributivity

T5' Complements

T1 Identity

T11: Consensus

Number	Theorem	Name
T11	$(B \bullet C) + (\bar{B} \bullet D) + (C \bullet D) =$ $(B \bullet C) + (\bar{B} \bullet D)$	Consensus

Prove using other theorems and axioms:

T11: Consensus

Number	Theorem	Name
T11	$(B \bullet C) + (\bar{B} \bullet D) + (C \bullet D) = (B \bullet C) + (\bar{B} \bullet D)$	Consensus

Prove using other theorems and axioms:

$$\begin{aligned} & \mathbf{B \bullet C + \bar{B} \bullet D + C \bullet D} \\ &= BC + \bar{B}D + (CDB + C\bar{D}B) \\ &= BC + \bar{B}D + \bar{B}CD + BCD \\ &= BC + BCD + \bar{B}D + \bar{B}CD \\ &= (BC + BCD) + (\bar{B}D + \bar{B}CD) \\ &= BC + \bar{B}D \end{aligned}$$

T10: Combining
T6: Commutativity
T6: Commutativity
T7: Associativity
T9': Covering

Boolean Theorems of Several Vars

#	Theorem	Dual	Name
T6	$B \bullet C = C \bullet B$	$B + C = C + B$	Commutativity
T7	$(B \bullet C) \bullet D = B \bullet (C \bullet D)$	$(B + C) + D = B + (C + D)$	Associativity
T8	$B \bullet (C + D) = (B \bullet C) + (B \bullet D)$	$B + (C \bullet D) = (B + C) (B + D)$	Distributivity
T9	$B \bullet (B + C) = B$	$B + (B \bullet C) = B$	Covering
T10	$(B \bullet C) + (B \bullet \bar{C}) = B$	$(B + C) \bullet (B + \bar{C}) = B$	Combining
T11	$(B \bullet C) + (\bar{B} \bullet D) + (C \bullet D) = (B \bullet C) + (\bar{B} \bullet D)$	$(B + C) \bullet (\bar{B} + D) \bullet (C + D) = (B + C) \bullet (\bar{B} + D)$	Consensus

Simplification methods

- **Distributivity (T8, T8')**

$$B(C+D) = BC + BD$$

$$B + CD = (B+C)(B+D)$$
- **Covering (T9')**

$$A + AP = A$$
- **Combining (T10)**

$$P\bar{A} + PA = P$$
- **Expansion**

$$P = P\bar{A} + PA$$

$$A = A + AP$$
- **Duplication**

$$A = A + A$$
- **“Simplification” theorem**

$$P\bar{A} + A = P + A$$

$$PA + \bar{A} = P + \bar{A}$$



Simplifying Boolean Equations

Example 1:

$$Y = A\bar{B} + AB$$

Simplifying Boolean Equations

Example 1:

$$Y = A\bar{B} + AB$$

$$Y = A$$

T10: Combining

or

$$= A(\bar{B} + B)$$

T8: Distributivity

$$= A(1)$$

T5': Complements

$$= A$$

T1: Identity



Simplification methods

- **Distributivity (T8, T8')**

$$B(C+D) = BC + BD$$

$$B + CD = (B+C)(B+D)$$
- **Covering (T9')**

$$A + AP = A$$
- **Combining (T10)**

$$P\bar{A} + PA = P$$
- **Expansion**

$$P = P\bar{A} + PA$$

$$A = A + AP$$
- **Duplication**

$$A = A + A$$
- **“Simplification” theorem**

$$P\bar{A} + A = P + A$$

$$PA + \bar{A} = P + \bar{A}$$



Simplifying Boolean Equations

Example 2:

$$Y = A(AB + ABC)$$

Simplifying Boolean Equations

Example 2:

$$Y = A(AB + ABC)$$

$$= A(AB(1 + C))$$

$$= A(AB(1))$$

$$= A(AB)$$

$$= (AA)B$$

$$= AB$$

T8: Distributivity

T2': Null Element

T1: Identity

T7: Associativity

T3: Idempotency

Simplification methods

- **Distributivity (T8, T8')**

$$B(C+D) = BC + BD$$

$$B + CD = (B+C)(B+D)$$
- **Covering (T9')**

$$A + AP = A$$
- **Combining (T10)**

$$P\bar{A} + PA = P$$
- **Expansion**

$$P = P\bar{A} + PA$$

$$A = A + AP$$
- **Duplication**

$$A = A + A$$
- **“Simplification” theorem**

$$P\bar{A} + A = P + A$$

$$PA + \bar{A} = P + \bar{A}$$



Simplifying Boolean Equations

Example 3:

$$Y = A'BC + A'$$

$$\text{Recall: } A' = \overline{A}$$

Simplifying Boolean Equations

Example 3:

$$Y = A'BC + A'$$

$$\text{Recall: } A' = \bar{A}$$

Note:

- A' is shorthand for \bar{A} .
- But use the tick symbol (') **only when typing**.
- It's easy to lose ticks (') when writing by hand!
- It is strongly recommended that you simplify equations by writing by hand.



Simplifying Boolean Equations

Example 3:

$$Y = A'BC + A'$$

$$= A'$$

or

$$= A'(BC + 1)$$

$$= A'(1)$$

$$= A'$$

Recall: $A' = \overline{A}$

T9' Covering: $X + XY = X$

T8: Distributivity

T2': Null Element

T1: Identity



Simplifying Boolean Equations

Example 4:

$$Y = AB'C + ABC + A'BC$$

Simplification methods

- **Distributivity (T8, T8')**

$$B(C+D) = BC + BD$$

$$B + CD = (B+C)(B+D)$$
- **Covering (T9')**

$$A + AP = A$$
- **Combining (T10)**

$$P\bar{A} + PA = P$$
- **Expansion**

$$P = P\bar{A} + PA$$

$$A = A + AP$$
- **Duplication**

$$A = A + A$$
- **“Simplification” theorem**

$$P\bar{A} + A = P + A$$

$$PA + \bar{A} = P + \bar{A}$$



Simplifying Boolean Equations

Example 4:

$$Y = AB'C + ABC + A'BC$$

$$= AB'C + \mathbf{ABC} + \mathbf{ABC} + A'BC \quad \text{T3': Idempotency}$$

$$= (AB'C + ABC) + (ABC + A'BC) \quad \text{T7': Associativity}$$

$$= AC + BC \quad \text{T10: Combining}$$

Simplification methods

- **Distributivity (T8, T8')**

$$B(C+D) = BC + BD$$

$$B + CD = (B+ C)(B+D)$$
- **Covering (T9')**

$$A + AP = A$$
- **Combining (T10)**

$$P\bar{A} + PA = P$$
- **Expansion**

$$P = P\bar{A} + PA$$

$$A = A + AP$$
- **Duplication**

$$A = A + A$$
- **“Simplification” theorem**

$$P\bar{A} + A = P + A$$

$$PA + \bar{A} = P + \bar{A}$$



Simplifying Boolean Equations

Example 5:

$$Y = AB + BC + B'D' + AC'D'$$

Method 1:

$$\begin{aligned} Y &= AB + BC + B'D' + (ABC'D' + AB'C'D') \\ &= (AB + ABC'D') + BC + (B'D' + AB'C'D') \\ &= AB + BC + B'D' \end{aligned}$$

T10: Combining
T6: Commutativity
T7: Associativity
T9: Covering

Method 2:

$$\begin{aligned} Y &= AB + BC + B'D' + AC'D' + AD' \\ &= AB + BC + B'D' + AD' \\ &= AB + BC + B'D' \end{aligned}$$

T11: Consensus
T9: Covering
T11: Consensus

Simplification methods

• **Distributivity (T8, T8')**

$$B(C+D) = BC + BD$$

$$B + CD = (B + C)(B + D)$$

• **Covering (T9')**

$$A + AP = A$$

• **Combining (T10)**

$$\overline{PA} + PA = P$$

• **Expansion**

$$P = \overline{PA} + PA$$

$$A = A + AP$$

• **Duplication**

$$A = A + A$$

• **“Simplification” theorem**

$$\overline{PA} + A = P + A$$

$$PA + \overline{A} = P + \overline{A}$$

Simplifying Boolean Equations

Example 6:

$$Y = (A + BC)(A + DE)$$

Apply T8' first when possible: $W + XZ = (W + X)(W + Z)$

Simplifying Boolean Equations

Example 6:

$$Y = (A + BC)(A + DE)$$

Apply T8' first when possible: $W + XZ = (W + X)(W + Z)$

Make: $X = BC$, $Z = DE$ and rewrite equation

$Y = (A + X)(A + Z)$	substitution ($X = BC$, $Z = DE$)
$= A + XZ$	T8': Distributivity
$= A + BCDE$	substitution

or

$Y = AA + ADE + ABC + BCDE$	T8: Distributivity
$= A + ADE + ABC + BCDE$	T3: Idempotency
$= \mathbf{A} + \mathbf{ADE} + ABC + BCDE$	
$= \mathbf{A} + ABC + BCDE$	T9': Covering
$= A + BCDE$	T9': Covering

Simplifying Boolean Equations

Example 6:

$$Y = (A + BC)(A + DE)$$

Apply T8' first when possible: $W + XZ = (W + X)(W + Z)$

Make: $X = BC$, $Z = DE$ and rewrite equation

$Y = (A + X)(A + Z)$	substitution ($X = BC$, $Z = DE$)
$= A + XZ$	T8': Distributivity
$= A + BCDE$	substitution

or

$Y = AA + ADE + ABC + BCDE$	T8: Distributivity
$= A + ADE + ABC + BCDE$	T3: Idempotency
$= \mathbf{A} + \mathbf{ADE} + ABC + BCDE$	
$= \mathbf{A} + ABC + BCDE$	T9': Covering
$= A + BCDE$	T9': Covering

This is called ***multiplying out*** an expression to get sum-of-products (SOP) form.

Review: Canonical SOP & POS Forms

- SOP – sum-of-products**

O	C	E	minterm
0	0	0	$\overline{O} \overline{C}$
0	1	0	$\overline{O} C$
1	0	1	$O \overline{C}$
1	1	0	$O C$

$$E = O\overline{C}$$
$$= \Sigma(2)$$

- POS – product-of-sums**

O	C	E	maxterm
0	0	0	$O + C$
0	1	0	$O + \overline{C}$
1	0	1	$\overline{O} + C$
1	1	0	$\overline{O} + \overline{C}$

$$E = (O + C)(O + \overline{C})(\overline{O} + \overline{C})$$
$$= \Pi(0, 1, 3)$$

Multiplying Out: SOP Form

An expression is in **sum-of-products (SOP)** form when all products contain literals only.

- SOP form: $Y = AB + BC' + DE$
- **NOT** SOP form: $Y = DF + E(A' + B)$
- SOP form: $Z = A + BC + DE'F$

Multiplying Out: SOP Form

Example:

$$Y = (A + C + D + E)(A + B)$$

Apply T8' first when possible: $W + XZ = (W + X)(W + Z)$

Make: $X = (C + D + E)$, $Z = B$ and rewrite equation

$$Y = (A + X)(A + Z)$$

substitution ($X = (C + D + E)$, $Z = B$)

$$= A + XZ$$

T8': Distributivity

$$= A + (C + D + E)B$$

substitution

$$= A + BC + BD + BE$$

T8: Distributivity

or

$$Y = AA + AB + AC + BC + AD + BD + AE + BE$$

T8: Distributivity

$$= A + AB + AC + AD + AE + BC + BD + BE$$

T3: Idempotency

$$= A + BC + BD + BE$$

T9': Covering



Factoring: POS Form

An expression is in **product-of-sums (POS)** form when all sums contain literals only.

- POS form: $Y = (A+B)(C+D)(E'+F)$
- **NOT** POS form: $Y = (D+E)(F'+GH)$
- POS form: $Z = A(B+C)(D+E')$

Canonical POS form: each product contains 1 of each literal.



Factoring: POS Form

Example 1:

$$Y = (A + B' C D E)$$

Apply T8' first when possible: $W + XZ = (W + X)(W + Z)$

Make: $X = B'C$, $Z = DE$ and rewrite equation

$$Y = (A + XZ)$$

substitution ($X = B'C$, $Z = DE$)

$$= (A + B'C)(A + DE)$$

T8': Distributivity

$$= (A + B')(A + C)(A + D)(A + E)$$

T8': Distributivity

Factoring: POS Form

Example 2:

$$Y = AB + C'DE + F$$

Apply T8' first when possible: $W+XZ = (W+X)(W+Z)$

Make: $W = AB$, $X = C'$, $Z = DE$ and rewrite equation

$$\begin{aligned} Y &= (W+XZ) + F && \text{substitution } W = AB, X = C', Z = DE \\ &= (W+X)(W+Z) + F && \text{T8': Distributivity} \\ &= (AB+C')(AB+DE)+F && \text{substitution} \\ &= (A+C')(B+C')(AB+D)(AB+E)+F && \text{T8': Distributivity} \\ &= (A+C')(B+C')(A+D)(B+D)(A+E)(B+E)+F && \text{T8': Distributivity} \\ &= (A+C'+F)(B+C'+F)(A+D+F)(B+D+F)(A+E+F)(B+E+F) && \text{T8': Distributivity} \end{aligned}$$

DeMorgan's Theorem

Number	Theorem	Name
T12	$\overline{B_0 \bullet B_1 \bullet B_2 \dots} = \overline{B_0} + \overline{B_1} + \overline{B_2} \dots$	DeMorgan's Theorem

DeMorgan's Theorem

Number	Theorem	Name
T12	$\overline{B_0 \bullet B_1 \bullet B_2 \dots} = \overline{B_0} + \overline{B_1} + \overline{B_2} \dots$	DeMorgan's Theorem

The **complement** of the **product**
is the
sum of the **complements**

DeMorgan's Theorem: Dual

#	Theorem	Dual	Name
T12	$\overline{B_0 \bullet B_1 \bullet B_2 \dots} = \overline{B_0} + \overline{B_1} + \overline{B_2} \dots$	$\overline{B_0 + B_1 + B_2 \dots} = \overline{B_0} \bullet \overline{B_1} \bullet \overline{B_2} \dots$	DeMorgan's Theorem



The **complement** of the **product**
is the
sum of the **complements**.

Dual: The **complement** of the **sum**
is the
product of the **complements**.





DeMorgan's Theorem

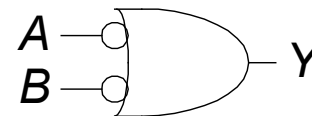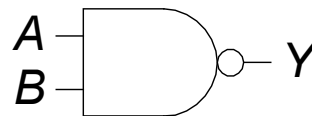- $Y = \overline{AB} = \overline{A} + \overline{B}$



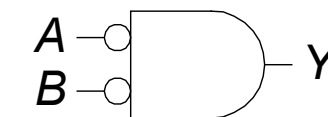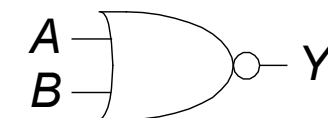- $Y = \overline{A + B} = \overline{A} \cdot \overline{B}$



DeMorgan's Theorem Example 1

$$Y = \overline{(A+BD)C}$$

DeMorgan's Theorem Example 1

$$\begin{aligned} Y &= \overline{(\overline{A + BD})\overline{C}} \\ &= \overline{(\overline{A + BD})} + \overline{\overline{C}} \\ &= (\overline{A} \bullet \overline{(\overline{BD})}) + C \\ &= (\overline{A} \bullet (BD)) + C \\ &= \overline{A}BD + C \end{aligned}$$

DeMorgan's Theorem Example 2



$$Y = \overline{(\overline{ACE} + \overline{D})} + B$$

DeMorgan's Theorem Example 2



$$\begin{aligned}
 Y &= \overline{(\overline{ACE + D})} + B \\
 &= (\overline{ACE + D}) \bullet \overline{B} \\
 &= (\overline{ACE} \bullet \overline{D}) \bullet \overline{B} \\
 &= ((\overline{AC} + \overline{E}) \bullet D) \bullet \overline{B} \\
 &= ((AC + \overline{E}) \bullet D) \bullet \overline{B} \\
 &= (ACD + D\overline{E}) \bullet \overline{B} \\
 &= \overline{A}BCD + \overline{B}D\overline{E}
 \end{aligned}$$

DeMorgan's Theorem

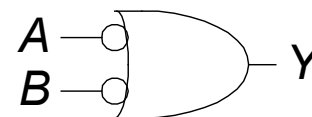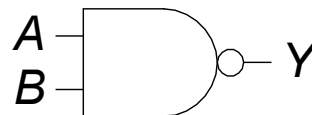- $Y = \overline{AB} = \overline{A} + \overline{B}$



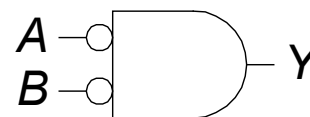
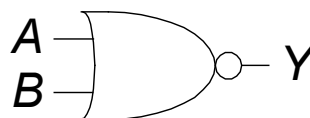
- $Y = \overline{A + B} = \overline{A} \cdot \overline{B}$



Bubble Pushing



- **Backward:**

- Body changes
- Adds bubbles to inputs

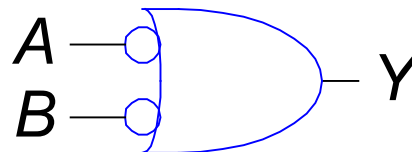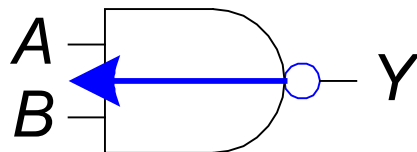


- **Forward:**

- Body changes
- Adds bubble to output

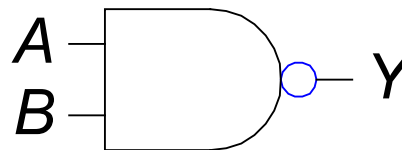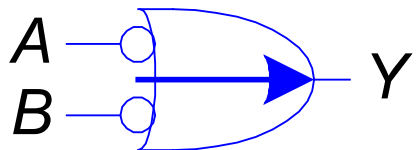


Bubble Pushing

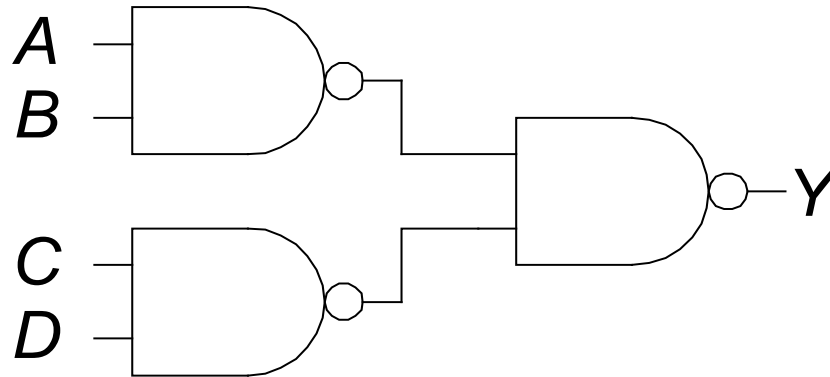- What is the Boolean expression for this circuit?



Bubble Pushing

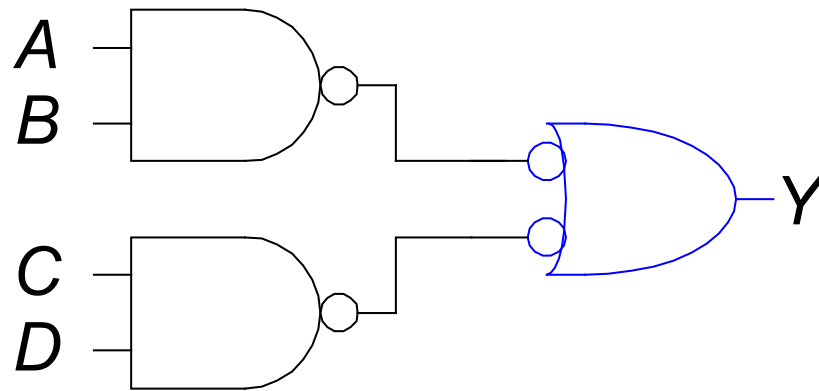
- What is the Boolean expression for this circuit?




$$Y = AB + CD$$

Bubble Pushing Rules

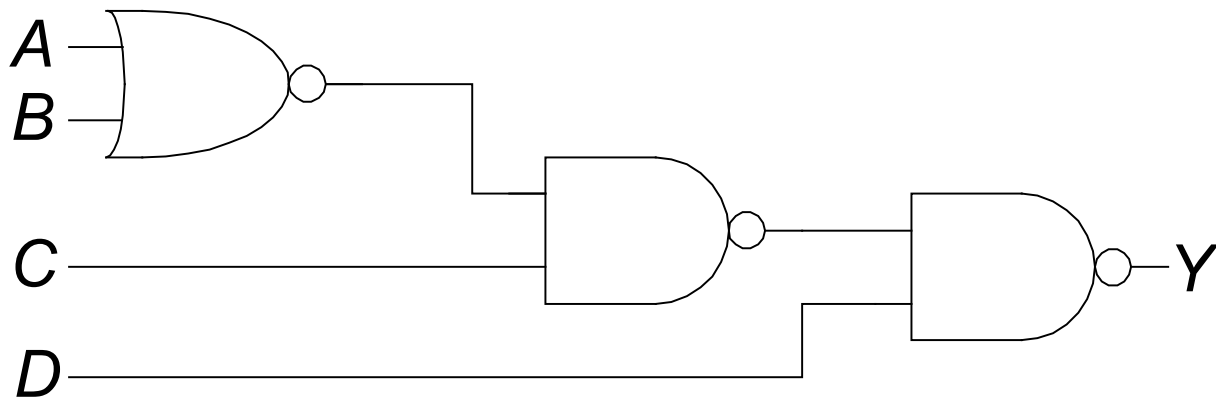
- Begin at output, then work toward inputs
- Push bubbles on final output back
- Draw gates in a form so bubbles cancel





Bubble Pushing Example

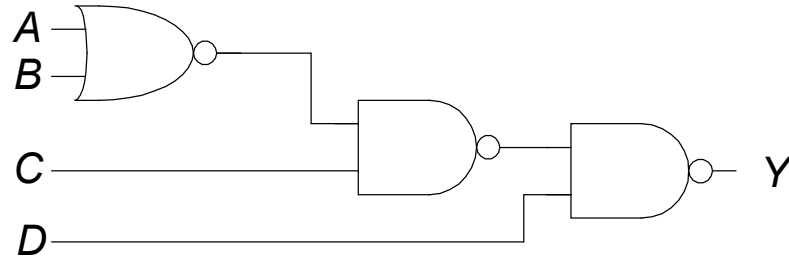




Bubble Pushing Example

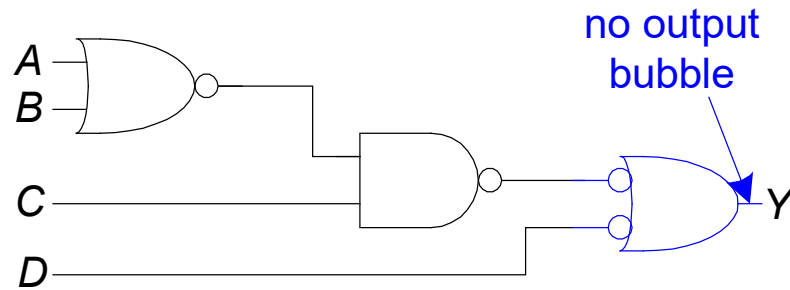

Bubble Pushing Example

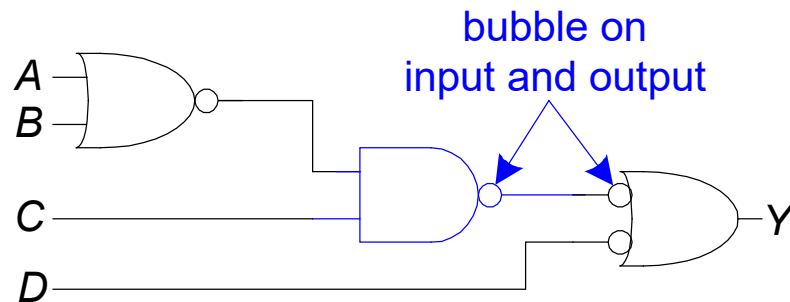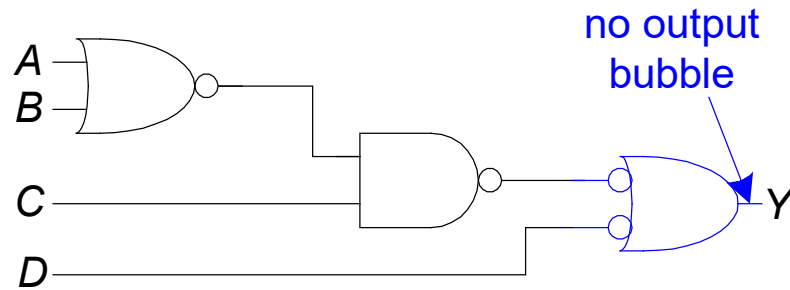


Bubble Pushing Example

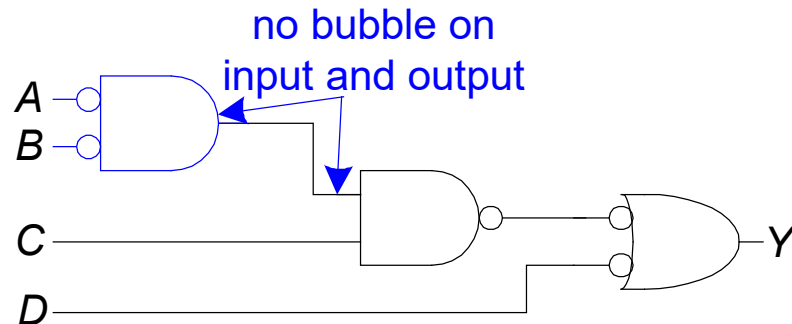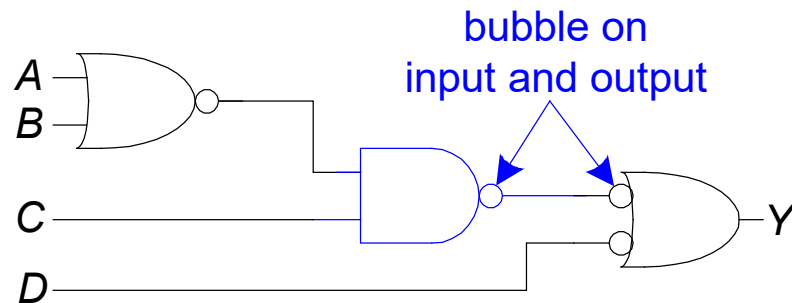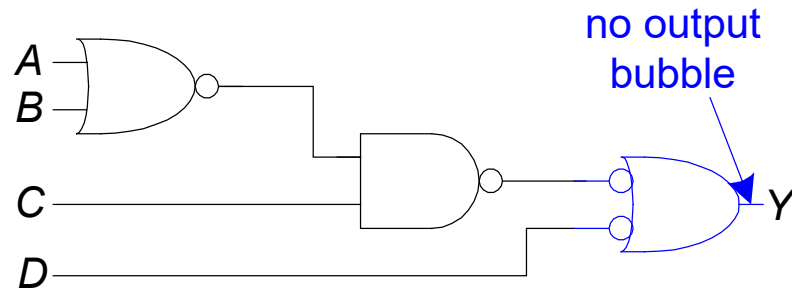

$$Y = \overline{A} \overline{B} C + \overline{D}$$

From Logic to Gates

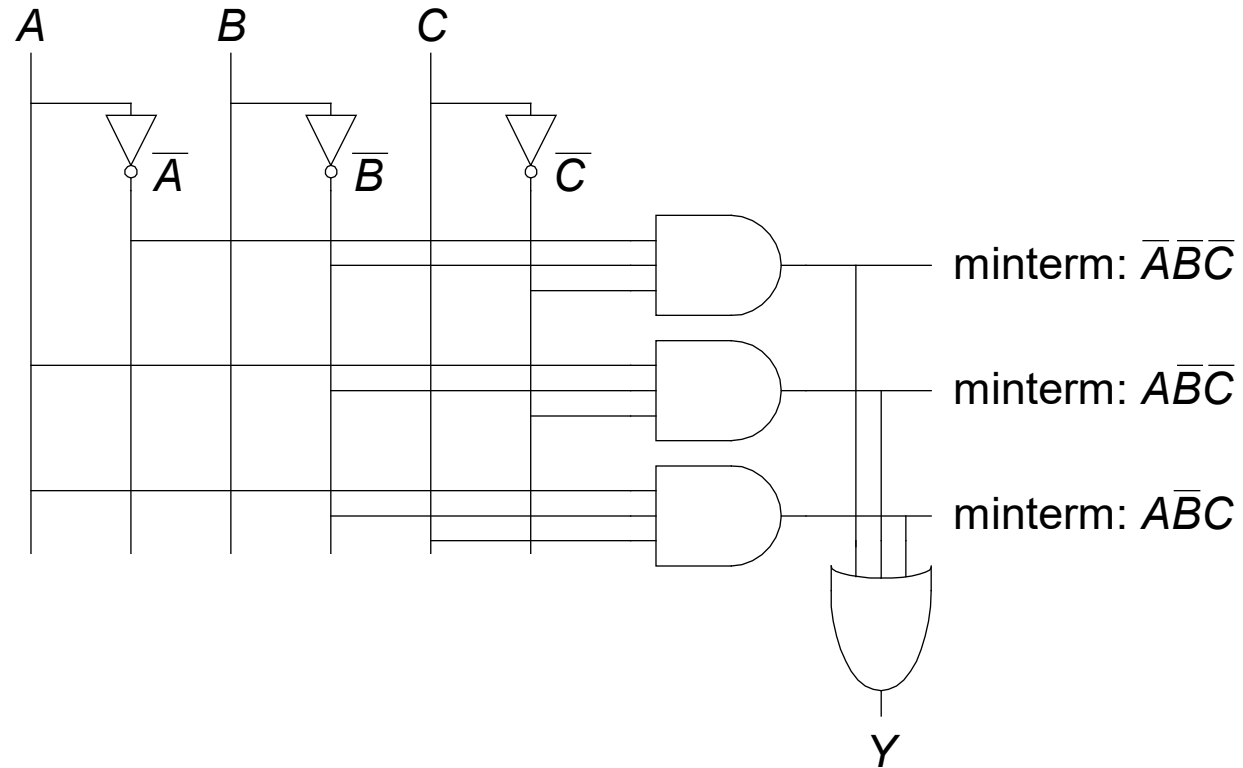- Two-level logic: ANDs followed by ORs
- Example: $Y = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + A\bar{B}C$




Circuit Schematics Rules

- Inputs on the left (or top)
- Outputs on right (or bottom)
- Gates flow from left to right
- Straight wires are best


Circuit Schematic Rules (cont.)

- Wires always connect at a T junction
- A dot where wires cross indicates a connection between the wires
- Wires crossing *without* a dot make no connection


wires connect
at a T junction

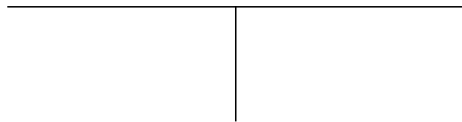

wires connect
at a dot

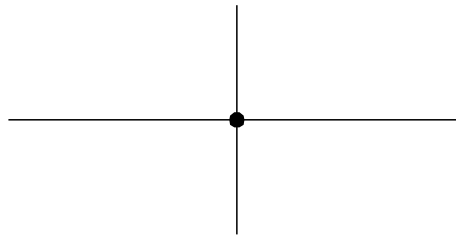

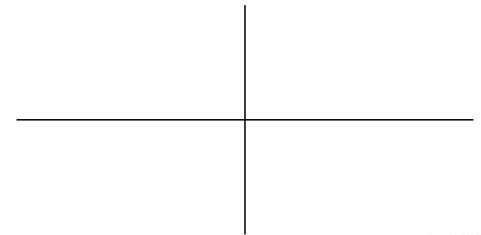
wires crossing
without a dot do
not connect



Multiple-Output Circuits

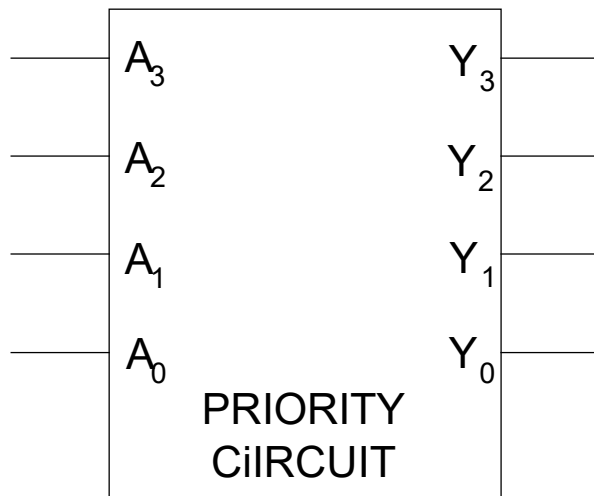- Example: Priority Circuit**

Output asserted
corresponding to
most significant
TRUE input




A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0				
0	0	0	1				1
0	0	1	0			1	
0	0	1	1			1	
0	1	0	0		1		
0	1	0	1		1		
0	1	1	0		1		
0	1	1	1		1		
1	0	0	0	1			
1	0	0	1	1			
1	0	1	0	1			
1	0	1	1	1			
1	1	0	0	1			
1	1	0	1	1			
1	1	1	0	1			
1	1	1	1	1			
1	1	1	1	1			

Multiple-Output Circuits

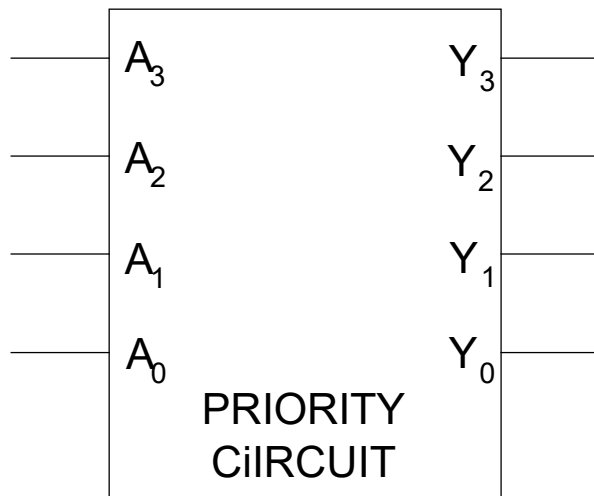- Example: Priority Circuit**

Output asserted
corresponding to
most significant
TRUE input




A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0
1	1	1	1	1	0	0	0



Priority Circuit Hardware

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

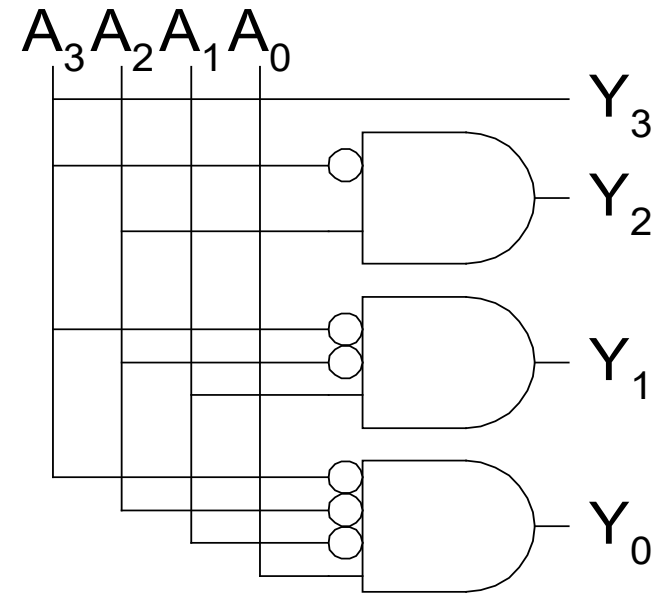


Don't Cares

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	X	0	0	1	0
0	1	X	X	0	1	0	0
1	X	X	X	1	0	0	0

Contention: X

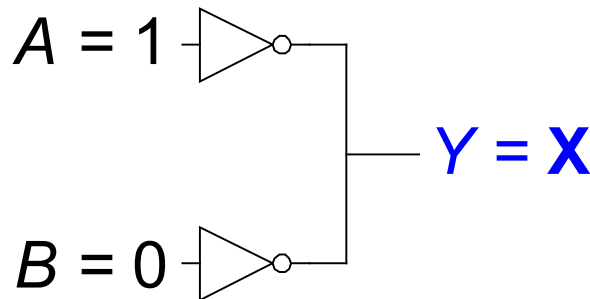- Contention: circuit tries to drive output to 1 **and** 0
 - Actual value somewhere in between
 - Could be 0, 1, or in forbidden zone
 - Might change with voltage, temperature, time, noise
 - Often causes excessive power dissipation




- **Warnings:**
 - Contention usually indicates a **bug**.
 - **X** is used for “don’t care” and contention - look at the context to tell them apart

Floating: Z

- Floating, high impedance, open, high Z
- Floating output might be 0, 1, or somewhere in between
 - A voltmeter won't indicate whether a node is floating


Tristate Buffer

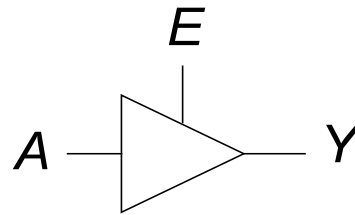

E	A	Y
0	0	Z
0	1	Z
1	0	0
1	1	1

Tristate Busses

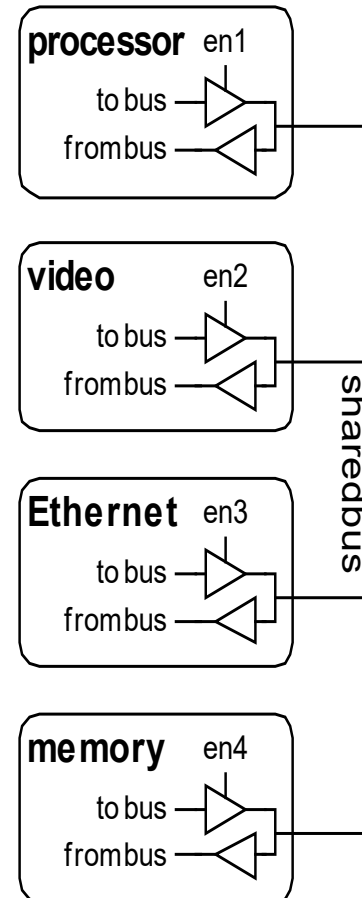- Floating nodes are used in tristate busses
 - Many different drivers
 - Exactly one is active at once



Karnaugh Maps (K-Maps)

- Boolean expressions can be minimized by combining terms
- K-maps minimize equations graphically
- $PA + P\bar{A} = P$

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

		AB			
		00	01	11	10
Y	C	0	1	0	0
	1	1	0	0	0

		AB			
		00	01	11	10
Y	C	0	$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$A\bar{B}\bar{C}$
	1	$\bar{A}\bar{B}C$	$\bar{A}BC$	ABC	$A\bar{B}C$

K-Map

- Circle 1's in adjacent squares
- In Boolean expression, include only literals whose true **and** complement form are **not** in the circle

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

		AB			
C	Y	00	01	11	10
	0	1	0	0	0
	1	1	0	0	0

$$Y = \overline{A}\overline{B}$$

3-Input K-Map

Y C \ AB		00	01	11	10
		0	1	1	0
C	0	$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$AB\bar{C}$	$A\bar{B}\bar{C}$
	1	$\bar{A}\bar{B}C$	$\bar{A}BC$	ABC	$A\bar{B}C$

Truth Table

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

K-Map

Y C \ AB		00	01	11	10
		0	1	1	0
C	0				
	1				

3-Input K-Map

Y C		AB			
		00	01	11	10
0	0	$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$A\bar{B}\bar{C}$	$AB\bar{C}$
	1	$\bar{A}\bar{B}C$	$\bar{A}BC$	ABC	$A\bar{B}C$

Truth Table

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

K-Map

Y C		AB			
		00	01	11	10
0	0	0	1	0	0
	1	0	1	1	0

$$Y = \bar{A}B + BC$$

K-Map Definitions

- **Complement:** variable with a bar over it
 $\bar{A}, \bar{B}, \bar{C}$
- **Literal:** variable or its complement
 $\bar{A}, A, \bar{B}, B, C, \bar{C}$
- **Implicant:** product of literals
 $\bar{A}\bar{B}C, \bar{A}C, BC$
- **Prime implicant:** implicant corresponding to the largest circle in a K-map

K-Map Rules

- **Every 1 must be circled** at least once
- Each circle must span a **power of 2** (i.e. 1, 2, 4) squares in each direction
- Each circle must be as **large** as possible
- A circle may **wrap around the edges**
- Circle a “**don't care**” (X) **only if it helps** minimize the equation

4-Input K-Map

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

		AB			
		00	01	11	10
CD	00				
	01				
	11				
	10				

4-Input K-Map

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

Y CD \ AB				
	00	01	11	10
00	1	0	0	1
01	0	1	0	1
11	1	1	0	0
10	1	1	0	1

4-Input K-Map

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

		AB			
Y	CD	00	01	11	10
	00	1	0	0	1
	01	0	1	0	1
	11	1	1	0	0
	10	1	1	0	1

$$Y = \bar{A}C + \bar{A}BD + A\bar{B}\bar{C} + \bar{B}\bar{D}$$

K-Maps with Don't Cares

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	X
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

		AB			
Y	CD	00	01	11	10
	00				
	01				
	11				
	10				

K-Maps with Don't Cares

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	X
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

		AB			
Y	CD	00	01	11	10
	00	1	0	X	1
	01	0	X	X	1
	11	1	1	X	X
	10	1	1	X	X

K-Maps with Don't Cares

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	X
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

		AB			
Y	CD	00	01	11	10
		00	01	11	10
	00	1	0	X	1
	01	0	X	X	1
	11	1	1	X	X
	10	1	1	X	X

$$Y = A + \bar{B}\bar{D} + C$$


Combinational Building Blocks

- Multiplexers
- Decoders

Multiplexer (Mux)

- Selects between one of N inputs to connect to output
- $\log_2 N$ -bit select input – control input
- Example:

2:1 Mux

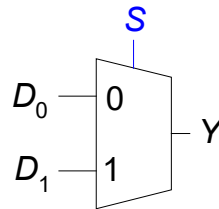

S	D_1	D_0	Y	S	Y
0	0	0	0	0	D_0
0	0	1	1	1	D_1
0	1	0	0		
0	1	1	1		
1	0	0	0		
1	0	1	0		
1	1	0	1		
1	1	1	1		


Multiplexer Implementations

- **Logic gates**

- Sum-of-products form


Y S	$D_0 D_1$			
	00	01	11	10
0	0	0	1	1
1	0	1	1	0

$$Y = D_0 \bar{S} + D_1 S$$

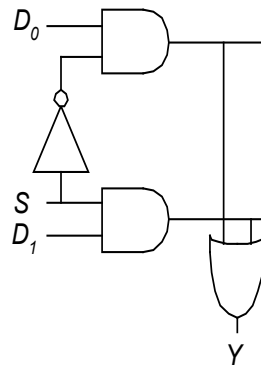

- **Tristates**

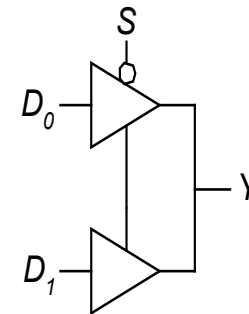- For an N-input mux, use N tristates
- Turn on exactly one to select the appropriate input




Logic using Multiplexers

Using the mux as a lookup table

<i>A</i>	<i>B</i>	<i>Y</i>
0	0	0
0	1	0
1	0	0
1	1	1

$$Y = AB$$

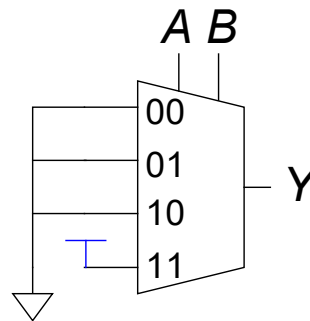


Logic using Multiplexers

Reducing the size of the mux


$$Y = AB$$

A	B	Y		A	Y
0	0	0	→	0	0
0	1	0			
1	0	0	→	1	B
1	1	1			

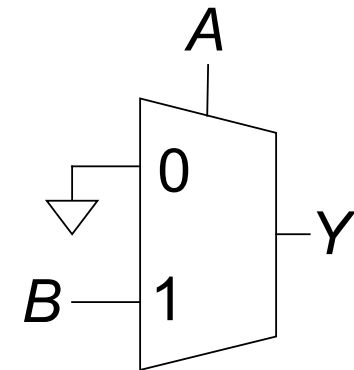


Decoders

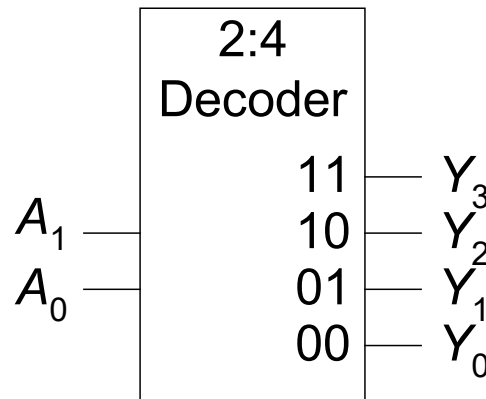- N inputs, 2^N outputs
- **One-hot** outputs: only **one output HIGH** at once




A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Decoder Implementation

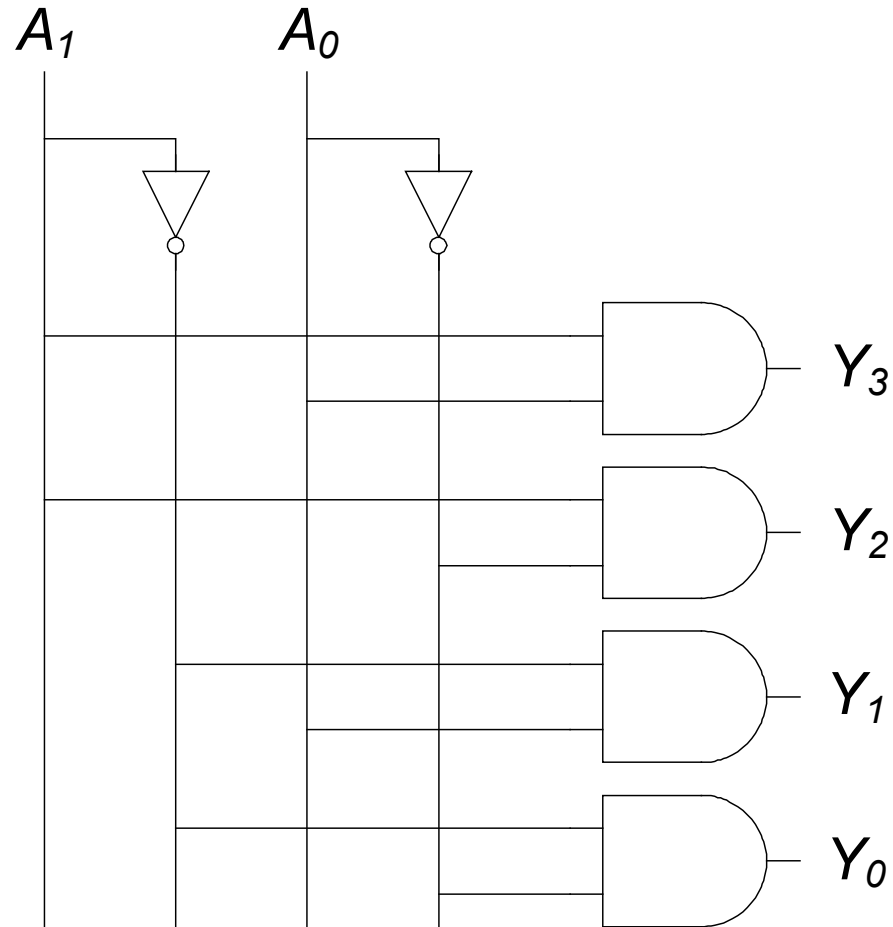


Logic Using Decoders

OR the minterms

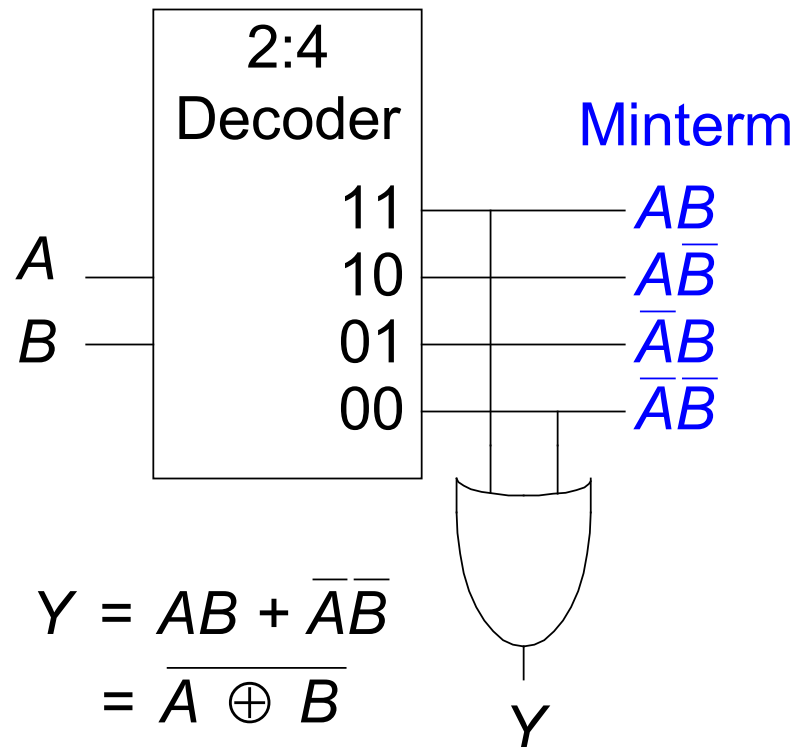


Timing

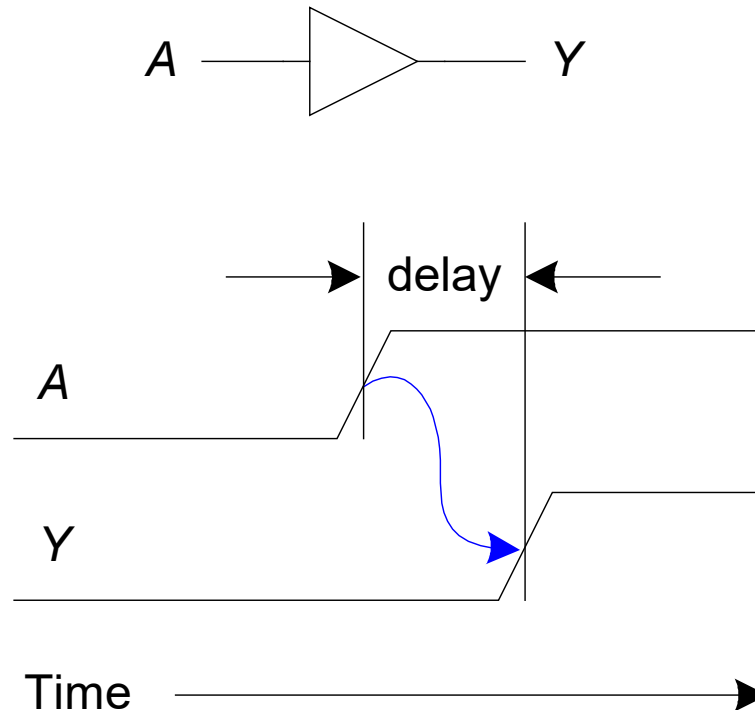- **Delay** between input change and output changing
- How to build fast circuits?



Propagation & Contamination Delay

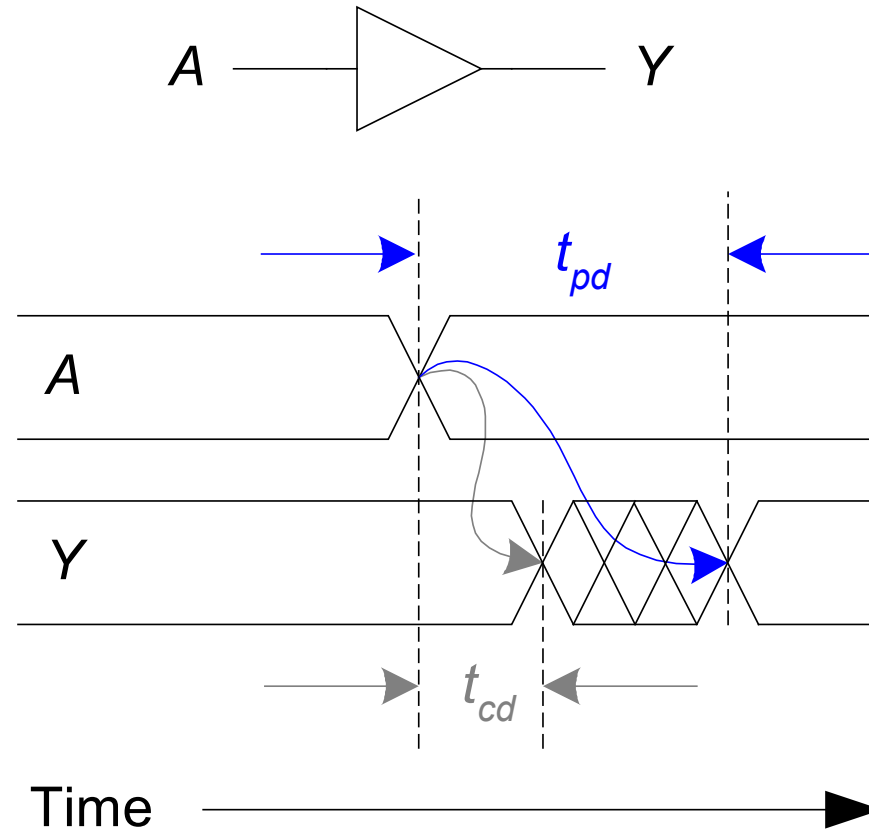- **Propagation delay:** t_{pd} = max delay from input to output
- **Contamination delay:** t_{cd} = min delay from input to output




Propagation & Contamination Delay

- **Delay is caused by**
 - Capacitance and resistance in a circuit
 - Speed of light limitation
- **Reasons why t_{pd} and t_{cd} may be different:**
 - Different rising and falling delays
 - Multiple inputs and outputs, some of which are faster than others
 - Circuits slow down when hot and speed up when cold



Critical (Long) & Short Paths

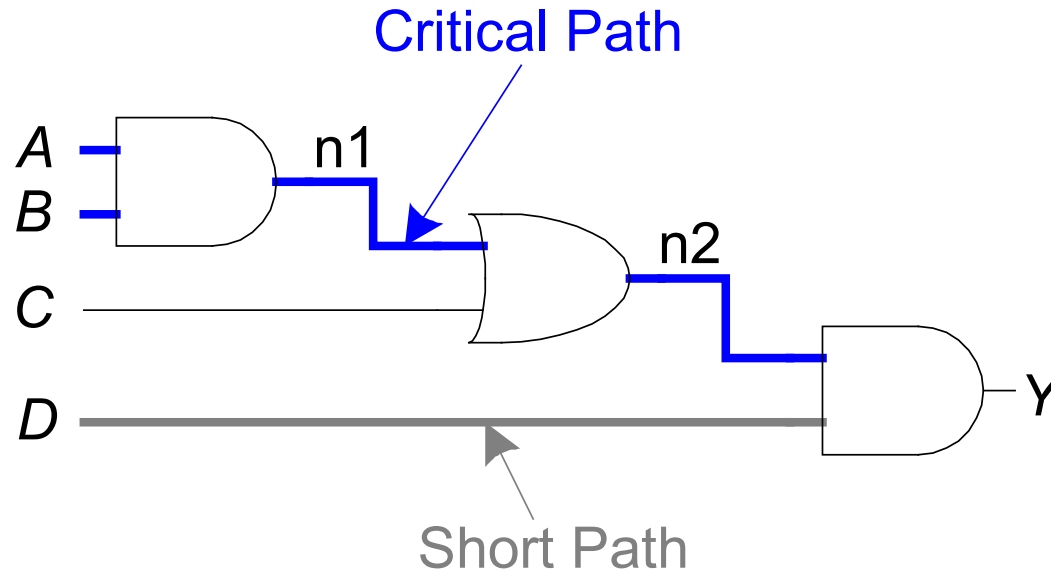

Critical (Long) Path: $t_{pd} = 2t_{pd_AND} + t_{pd_OR}$


Short Path: $t_{cd} = t_{cd_AND}$

Glitches

- When a single input change causes an output to change multiple times

Glitch Example


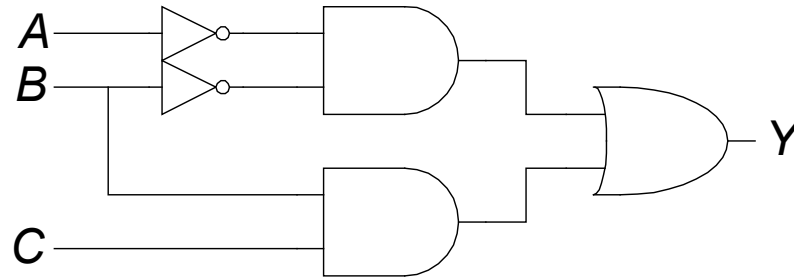
- What happens when $A = 0$, $C = 1$, B falls?





		AB			
		00	01	11	10
C	0	1	0	0	0
	1	1	1	1	0

$$Y = \bar{A}\bar{B} + BC$$

Glitch Example (cont.)

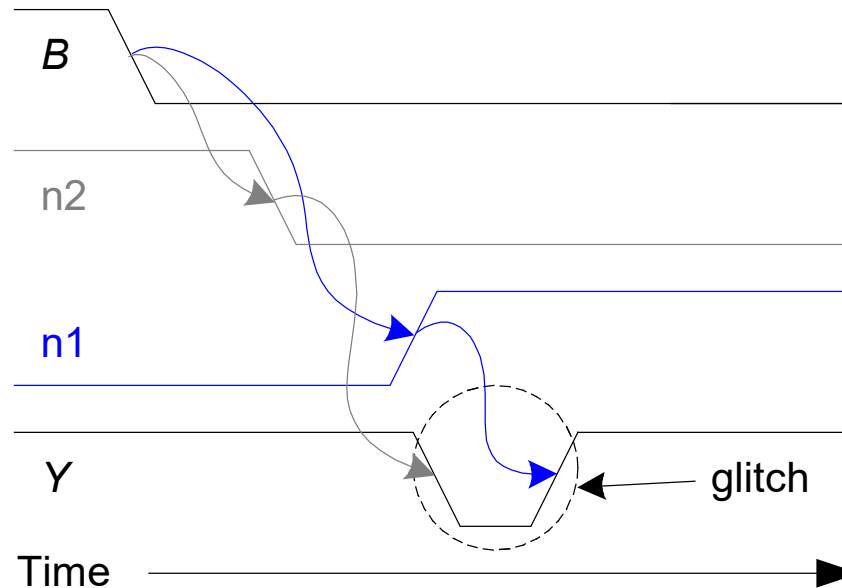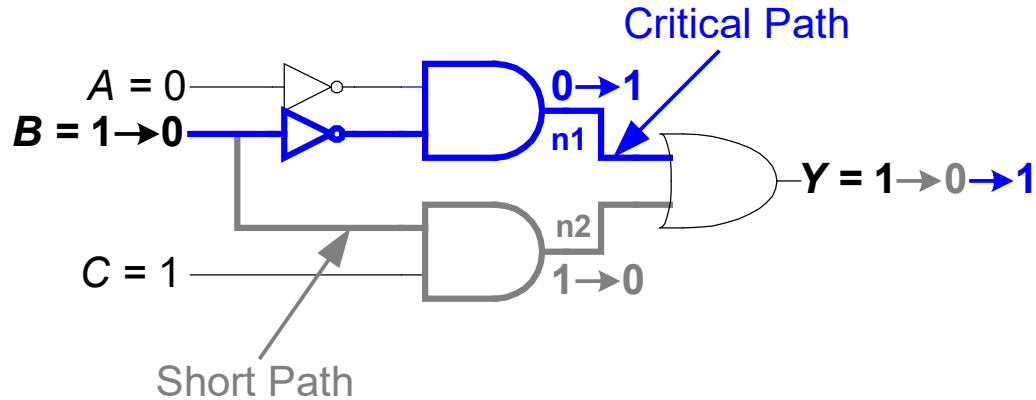

Fixing the Glitch

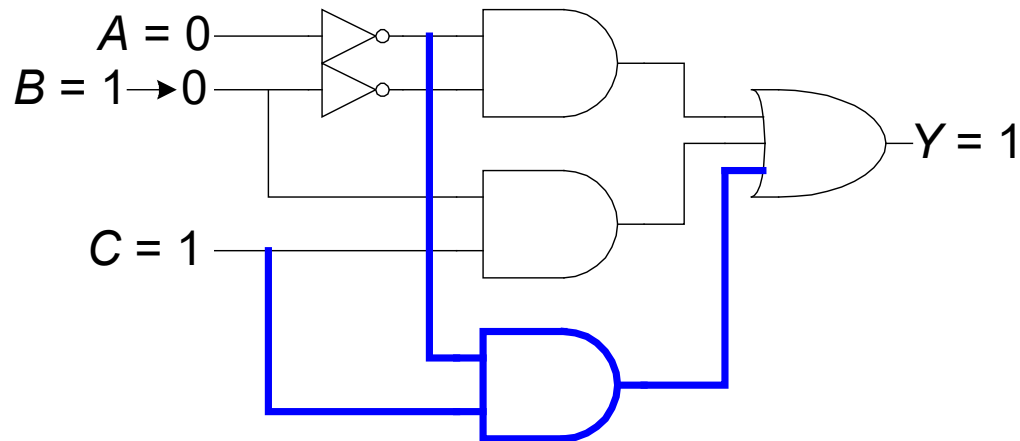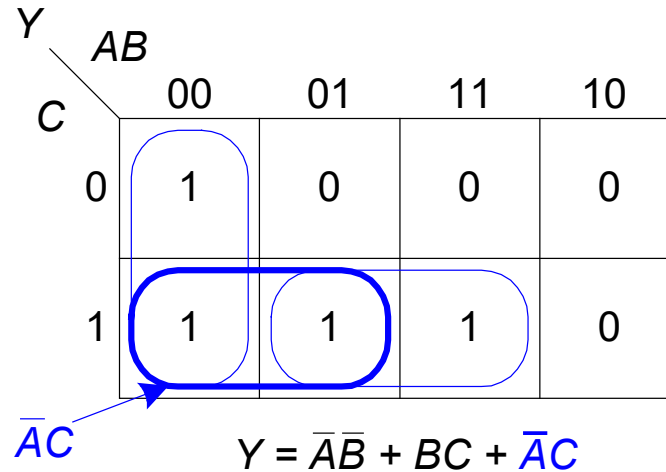

Why Understand Glitches?

- Because of **synchronous design** conventions (see Chapter 3), glitches don't cause problems.
- It's important to **recognize** a glitch: in simulations or on oscilloscope.
- We **can't get rid of all glitches** – simultaneous transitions on multiple inputs can also cause glitches.